

CprE 381: Computer Organization and Assembly-Level Programming

Project Part 1 Report


Team Members: _____ Ethan Roepke _____

_____ Ian Runestad _____

Project Teams Group #: _____ Group A_10 _____

Refer to the highlighted language in the project 1 instruction for the context of the following questions.

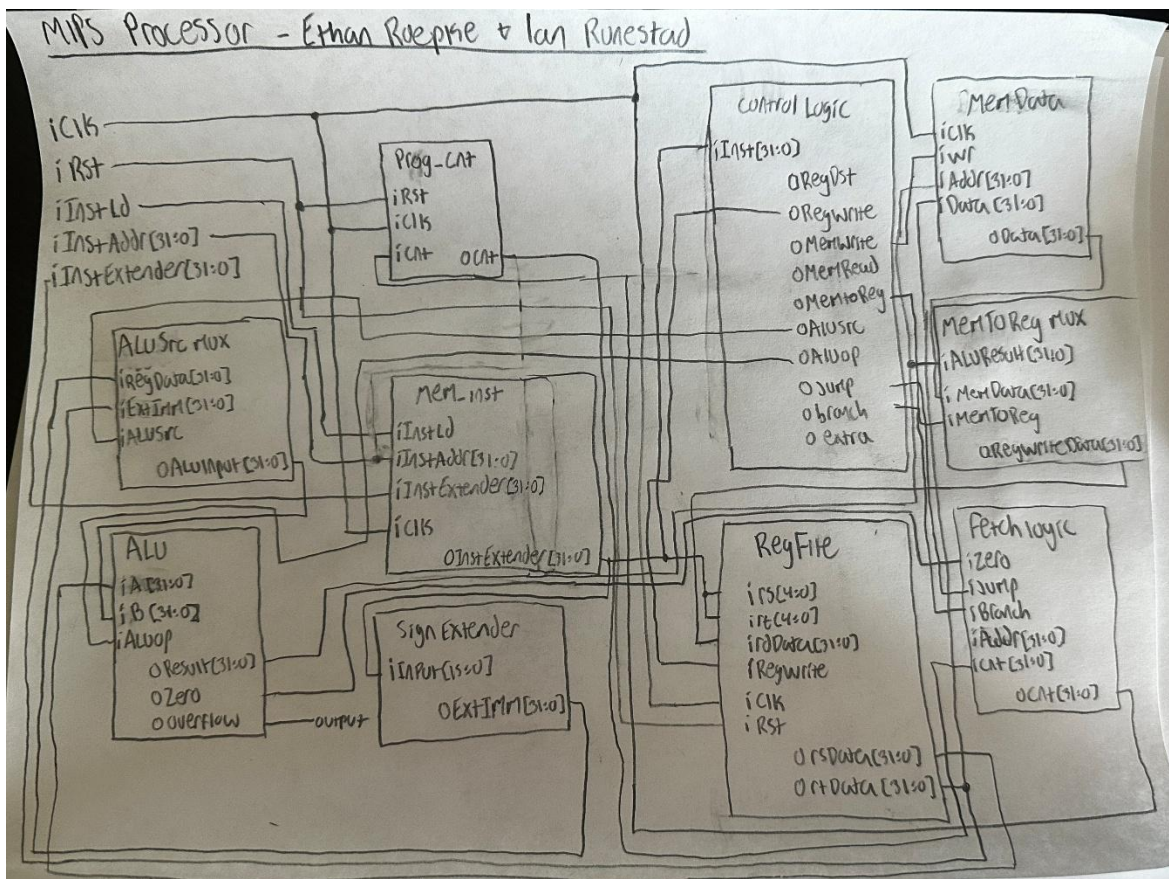[Part 1 (d)] Include your final MIPS processor schematic in your lab report.



[Part 2 (a.i)] Create a spreadsheet detailing the list of M instructions to be supported in your project alongside their binary opcodes and funct fields, if applicable. Create a separate column for each binary bit. Inside this spreadsheet, create a new column for the N control signals needed by your datapath implementation. The end result should be an $N \times M$ table where each row corresponds to the output of the control logic module for a given instruction.

| Instruction | Op5 | Op4 | Op3 | Op2 | Op1 | Op0 | Fun5 | Fun4 |
|-------------|-----|-----|-----|-----|-----|-----|------|------|
| add | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| sub | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| and | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| or | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| xor | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| sll | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| sll | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| srl | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| sra | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| lw | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| lh | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| lb | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| lhu | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| sw | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |
| beq | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| bne | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| addi | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| j | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| jal | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| halt | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |

[Part 2 (a.ii)] Implement the control logic module using whatever method and coding style you prefer. Create a testbench to test this module individually and show that your output matches the expected control signals from problem 1(a).

| Inputs | Op5 | Op4 | Op3 | Op2 | Op1 | Op0 | Fun5 | Fun4 |
|--------|-----|-----|-----|-----|-----|-----|------|------|
| add | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| sub | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| and | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| or | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| xor | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| sll | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| sll | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| srl | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| sra | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| lw | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| lh | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| lb | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| lhu | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| sw | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |
| beq | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| bne | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| addi | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| j | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| jal | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| halt | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |

- Normal Sequential Flow:
 - PC is updated as $PC = PC + 4$


- Used by most instructions like add, sub, lw, sw
- Unconditional Jump:
 - Updates PC with jump target: $PC = \{PC[31:28], \text{target}, 00\}$
 - Jump address is embedded in the instruction
- Jump and Link:
 - Same PC update as j: $PC = \{PC[31:28], \text{target}, 00\}$
 - Also saves return address ($PC + 4$) to register \$ra
- Jump Register:
 - PC is set to the value in a register: $PC = \$rs$
 - Requires reading a register for the next PC (resolved in Execute stage)
- Branch if Equal:
 - Conditional jump: if $\$rs == \rt , then $PC = PC + 4 + (\text{offset} \ll 2)$
 - Target is relative to current PC
- Branch if Not Equal:
 - Conditional jump: if $\$rs \neq \rt , then $PC = PC + 4 + (\text{offset} \ll 2)$
 - Also uses a relative offset

[Part 2 (b.i)] What are the control flow possibilities that your instruction fetch logic must support? Describe these possibilities as a function of the different control flow-related instructions you are required to implement.


- Sequential Execution:
 - Default case when no jump, branch, or register jump is active.
 - Fetch logic increments PC by 4 to fetch the next instruction.
- Unconditional Jump:
 - When $\text{JumpSelect} = 1$, fetch logic replaces PC with jump target address from instruction.
 - Target address is computed as $\{PC[31:28], \text{inst}[25:0], 00\}$.
- Branch Instructions:

- When BranchSelect = 1, fetch logic adds sign-extended and shifted xtendin (offset) to PC + 4.
 - Condition (zeroFlag or bne logic) determines if branch is taken.
 - If branch taken $\rightarrow PC = PC + 4 + (\text{offset} \ll 2)$.
 - If not taken $\rightarrow PC = PC + 4$.
- Jump Register:
 - When jrs = 1, fetch logic loads PC directly from register value JRin.
 - Overrides all other PC updates when active.

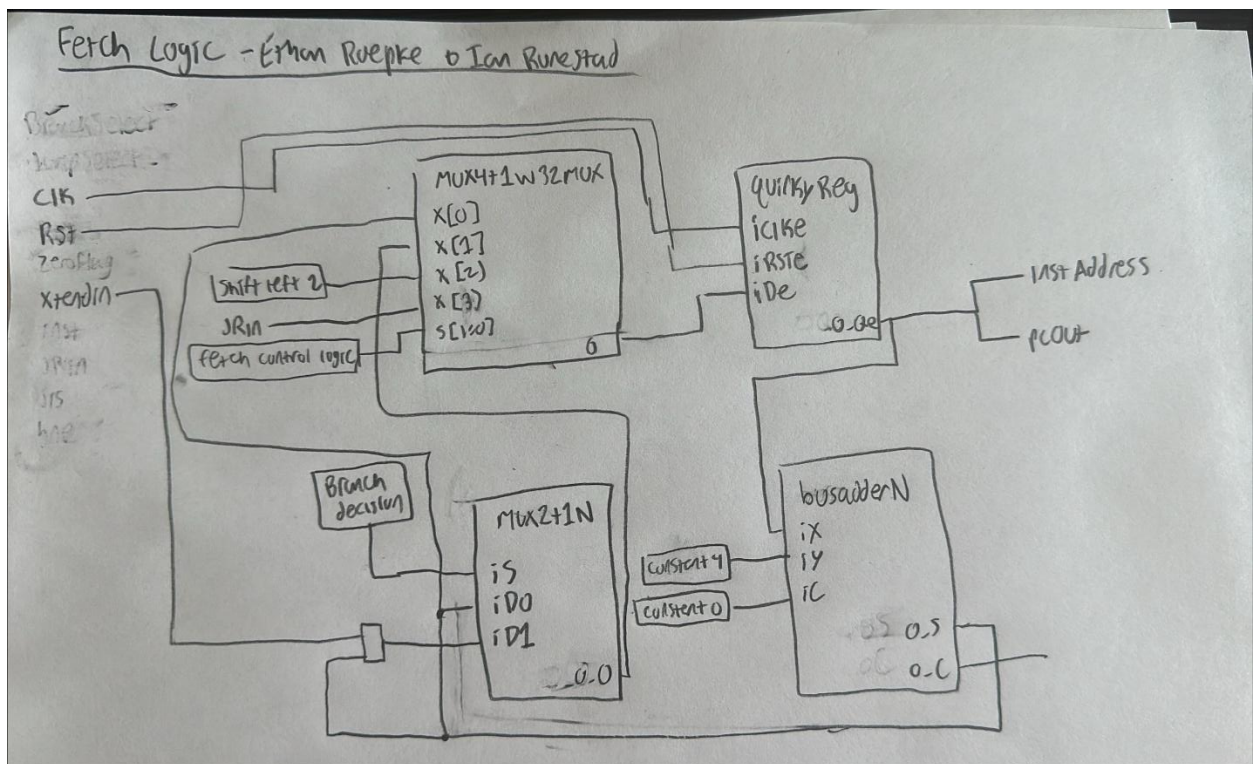[Part 2 (b.ii)] Draw a schematic for the instruction fetch logic and any other datapath modifications needed for control flow instructions. What additional control signals are needed?



 [Part 2 (b.iii)] Implement your new instruction fetch logic using VHDL. Use QuestaSim to test your design thoroughly to make sure it is working as expected. Describe how the execution of the control flow possibilities corresponds to the QuestaSim waveforms in your writeup.



- Initial Reset (`res = '1'`)
 - PC (`instAddress / pcOUT`) is held at 0.
 - No instruction fetch happens.
 - Confirms correct reset behavior.
- Sequential Execution (default case)
 - When `JumpSelect`, `BranchSelect`, and `jrs` are all '0', the PC increments by 4 each clock.
 - Waveform shows $PC = 0 \rightarrow 4 \rightarrow 8 \rightarrow 12$, etc.
 - Confirms $PC + 4$ progression.
- Jump Instruction (`JumpSelect = '1'`)
 - Jump target from `inst(25:0)` is used to compute jump address
 - PC jumps to 0x08, visible as a discontinuity in waveform.
 - Confirms correct jump operation.
- Branch Equal (`BranchSelect = '1'`, `zeroFlag = '1'`)
 - Branch is taken; offset (`xtendin`) is added to $PC+4$.
 - PC jump visible as skip ahead in waveform.
 - Confirms BEQ behavior.
- Branch Not Equal (`BranchSelect = '1'`, `bne = '1'`, `zeroFlag = '0'`)
 - Branch taken when zero flag is 0.
 - Offset added as in BEQ.

- PC jump by 8 shows in waveform.
- Confirms BNE behavior.
- Jump Register (jrs = '1')
 - PC is updated directly from JRin.
 - PC = 0x00000020 shows as abrupt jump in waveform.
 - Confirms JR support and direct control of PC.

[Part 2 (c.i.1)] Describe the difference between logical (`srl`) and arithmetic (`sra`) shifts. Why does MIPS not have a `sla` instruction?

In MIPS, the logical shift right and arithmetic shift right are two types of shift operations that differ in how they handle the sign bit during shifting. The SRL operation shifts the bits to the right while filling the leftmost bits with zeros regardless of the sign of the number. On the other hand, the SRA operation shifts the bits to the right as well, but it preserves the sign of the number by filling the leftmost bits with the sign bit. This makes the SRA suitable for signed values, ensuring that the result maintains the correct sign when performing the shift.

MIPS does not include a shift left arithmetic instruction because left shifts do not require special handling of the sign bit. When performing a shift left, all bits are moved to the left, and the rightmost bits are filled with zeros. This operation is identical for both signed and unsigned values, so there is no need for a separate arithmetic left shift instruction. The shift left logical operation, which is the equivalent of the SLA is enough for both signed and unsigned numbers.


[Part 2 (c.i.2)] In your writeup, briefly describe how your VHDL code implements both the arithmetic and logical shifting operations.

The VHDL code implements logical shifts by setting `lefty` to 0 and `fillSelect` to 0, filling vacated positions with 0s. Arithmetic shifts are implemented by setting `fillSelect` to 1, causing the vacated positions to be filled with the sign bit, preserving the number's sign. Both shifts use multiplexers to select the appropriate data path based on the shift amount and direction.

[Part 2 (c.i.3)] In your writeup, explain how the right barrel shifter above can be enhanced to also support left shifting operations.

To enhance the right barrel shifter to support left shifting, the lefty control signal can be used to determine the shift direction. When lefty is set to 0, the data will shift left; when lefty is set to 1, the data will shift right. The multiplexers would need to be adjusted to correctly handle left shifts, ensuring the vacated positions are filled with 0s for logical shifts or sign extended bits for arithmetic shifts. This allows the shifter to handle both left and right shifts based on the lefty signal.

[Part 2 (c.i.4)] Describe how the execution of the different shifting operations corresponds to the QuestaSim waveforms in your writeup.

 

Test 1: Logical Shift Left (LSL)

- Description: Shift ix = 0x00000001 left by 4 positions.
- Expected Result: oy = 0x00000010

Test 2: Logical Shift Right (LSR)

- Description: Shift ix = 0x00000010 right by 4 positions.
- Expected Result: oy = 0x00000001

Test 3: Arithmetic Shift Right (ASR)

- Description: Shift ix = 0x80000010 right by 4 positions (arithmetic shift).
- Expected Result: oy = 0xF0000001

Test 4: No Shift (Shift Count = 0)

- Description: No shift when shiftCount = 0.
- Expected Result: oy = 0x00000001

Test 5: Arithmetic Shift Left (ASL)

- Description: Shift ix = 0x00000001 left by 8 positions.
- Expected Result: oy = 0x01000000

Test 6: Maximal Shift (Shift Count = 31)

- Description: Shift ix = 0x00000001 by 31 positions.
- Expected Result: oy = 0x00000000

[Part 2 (c.ii.1)] In your writeup, briefly describe your design approach, including any resources you used to choose or implement the design. Include at least one design decision you had to make.

For the design of the ALU, we focused on creating a simple and efficient module capable of performing basic arithmetic and logical operations. One key design decision involved how to handle the Overflow and Carryout flags. These flags are essential for detecting errors in arithmetic operations, especially for signed numbers and shift operations. We used sign extension to detect overflow in addition and subtraction. We carefully managed the Carryout signal for addition and subtraction. The design utilized a multiplexer to select operations and a case statement to handle various ALU operations. Resources that we used includes, VHDL libraries and course provided ALU design examples.

[Part 2 (c.ii.2)] Describe how the execution of the different operations corresponds to the QuestaSim waveforms in your writeup.


Still need to do, unsure what to do here

[Part 2 (c.iii)] Draw a simplified, high-level schematic for the 32-bit ALU. Consider the following questions: how is Overflow calculated? How is Zero calculated? How is `slt` implemented?


Overflow is calculated during signed addition and subtraction by comparing the sign bits of the operands and the result. If the operands have the same sign but the result's sign is different, overflow occurs. This indicates that the result cannot be represented correctly in signed form.

Zero is calculated by checking if the ALU result is all zeros. If the entire 32-bit result is zero, the Zero flag is set to '1'; otherwise, it is '0'. This simple comparison is used to detect when an operation yields a zero value.

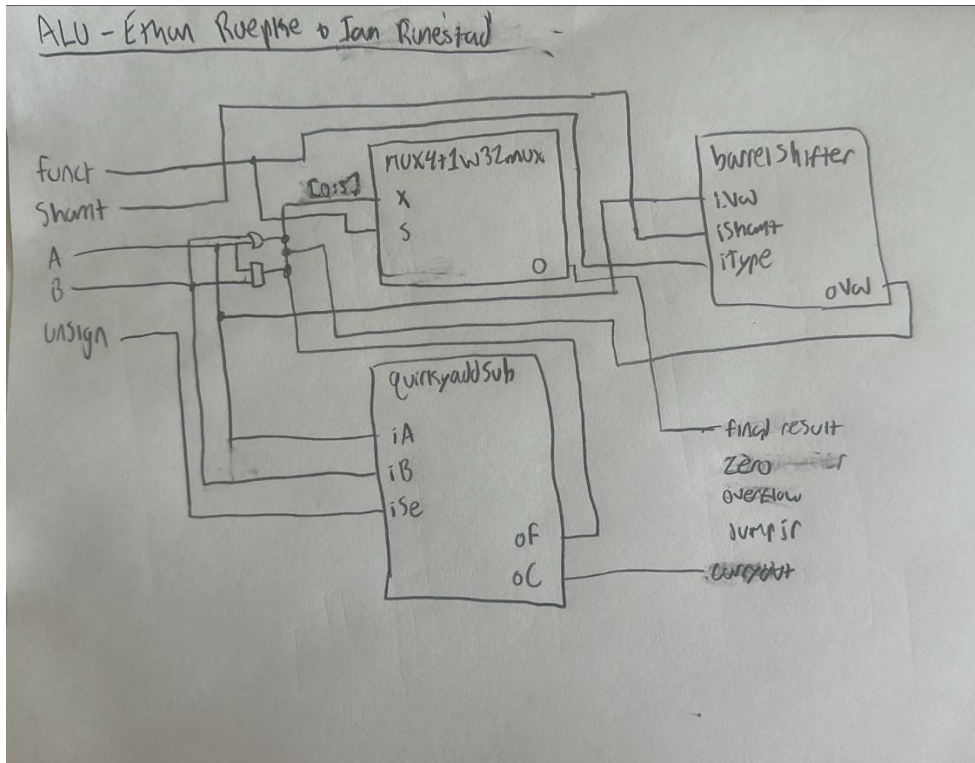SLT is implemented by subtracting B from A and checking the sign bit of the result. If the result is negative (sign bit is '1'), SLT outputs '1'; otherwise, it outputs '0'. This result is expanded into a 32-bit word with only the least significant bit set.



 [Part 2 (c.v)] Describe how the execution of the different operations corresponds to the QuestaSim waveforms in your writeup.



Tests 1-8 focuses on verifying the ALU's ability to perform addition and subtraction operations with both signed and immediate values, ensuring correct results and proper handling of overflow and carryout flags. Tests 9 and 10 evaluate the Set Less Than operation, ensuring the ALU correctly sets the result to 1 when A is less than B or the immediate value, and 0 otherwise. Tests 11 through 18 test the ALU's ability to perform bitwise operations such as AND, OR, XOR, and NOR, with immediate values to verify the


correctness of the bitwise results. Tests 19-24 focuses on shift operations, checking the ALU's ability to shift operands left or right by a specified amount, using the shift amount. Test 25 verifies the Zero flag, ensuring it is correctly set when the ALU operation results in a zero value. Test 26 evaluates the Overflow flag, particularly for unsigned arithmetic, to ensure that overflow is detected correctly when large values are involved. Finally, Test 27 validates the LUI operation, ensuring that the ALU correctly loads an immediate value into the upper 16 bits of the result.

[Part 2 (c.viii)] justify why your test plan is comprehensive. Include waveforms that demonstrate your test programs functioning.


The plan includes tests for arithmetic operations, logical operations, and shift operations which are fundamental to any processor. We have each operation being tested for correctness and special conditions like overflow, carryout, and zero flags. These are explicitly checked to ensure the ALU handles them properly. The addition of tests for flag handling ensures that the ALU behaves as expected under all conditions. The waveforms for these tests clearly demonstrate the ALU's correct operation with flags set as expected. This thorough testing of both normal and edge cases ensures that the ALU performs all its functions correctly and handles corner cases like overflow and zero values accurately.


[Part 3] In your writeup, show the QuestaSim output for each of the following tests, and provide a discussion of result correctness. It may be helpful to also annotate the waveforms directly.

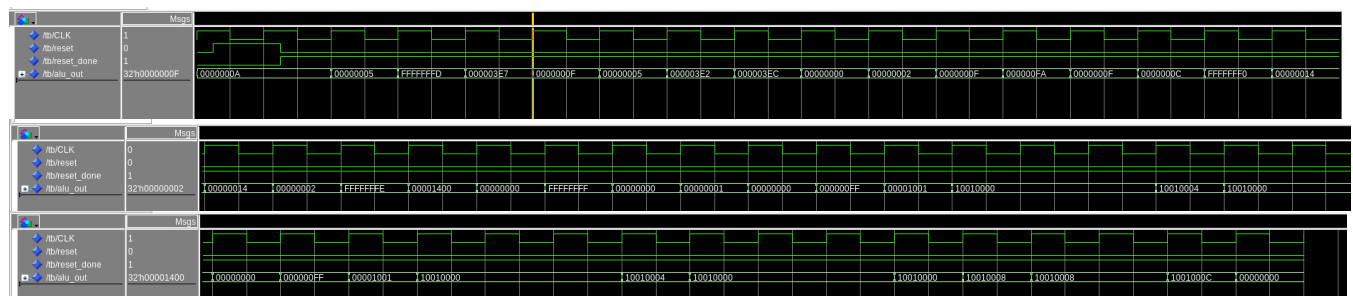[Part 3 (a)] Create a test application that makes use of every required arithmetic/logical instruction at least once. The application need not perform any particularly useful task, but it should demonstrate the full functionality of the processor (e.g., sequences of many instructions executed sequentially, 1 per cycle while data written into registers can be effectively retrieved and used by later instructions). Name this file Proj1_base_test.s.




 [Part 3 (b)] Create and test an application which uses each of the required control-flow instructions and has a call depth of at least 5 (i.e., the number of activation records on the stack is at least 4). Name this file Proj1_cf_test.s.



 

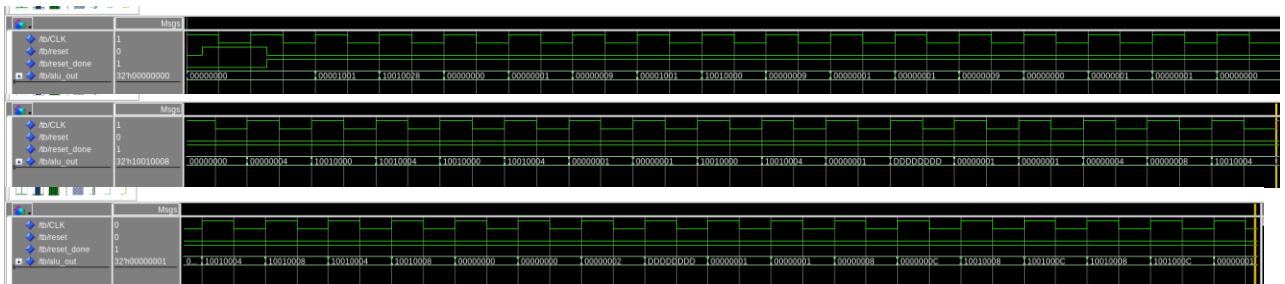[Part 3 (c)] Create and test an application that sorts an array with N elements using the BubbleSort algorithm ([link](#)). Name this file Proj1_bubblesort.s.



[Part 4] Report the maximum frequency your processor can run at and determine what your critical path is. Draw this critical path on top of your top-level schematic from part 1. What components would you focus on to improve the frequency?

Critical max frequency: 25.71mhz

Critical path:

PC (Program Counter) → Instruction Memory (IMem) → various multiplexers and ALU shifter → Data Memory (DMem) → final mux and logic → Register File (write input).

One critical area to address is the clock network delay, which contributes significantly to the overall timing. Optimizing the clock distribution network can help reduce this delay and improve the overall speed. Additionally, reducing delays in the memory accesses, particularly in components like the Instruction Memory and Data Memory will directly impact the critical path. This can be achieved by optimizing the read/write paths and ensuring faster memory access times. Another area of improvement is the multiplexers and registers, as they add incremental delays throughout the path. Streamlining the design of these elements can reduce their contribution to the overall path delay. Finally, minimizing the interconnect delay between these components, particularly in areas where the signal travels through several stages of interconnects, would further reduce the total critical path time and allow the processor to run at a higher frequency.

```

#
# CprE 381 toolflow Timing dump
#

```

FMax: 25.71mhz Clk Constraint: 20.00ns Slack: -18.89ns

The path is given below

```

=====
From Node   : fetch:cuffruffman|quirkyReg:PC|quirkydff:\regfile:5:reggie|s_Q
To Node     : regFile:reggie|registerNbit:\g1:12:dff|dffg:\regfile:24:reggie|s_Q
Launch Clock : iCLK
Latch Clock  : iCLK
Data Arrival Path:
Total (ns)  Incr (ns)  Type  Element
=====
0.000        0.000      launch edge time
3.066        3.066      R      clock network delay
3.298        0.232      uIco   fetch:cuffruffman|quirkyReg:PC|quirkydff:\regfile:5:reggie|s_Q
3.298        0.000      FF      CELL   cuffruffman|PC|\regfile:5:reggie|s_Q|q
3.674        0.376      FF      IC      s_IMemAddr[5]~6|datad
3.799        0.125      FF      CELL   s_IMemAddr[5]~6|combout
5.952        2.153      FF      IC      IMem|ram~42982|datad
6.377        0.425      FF      CELL   IMem|ram~42982|combout
6.605        0.228      FF      IC      IMem|ram~42983|datad
6.730        0.125      FF      CELL   IMem|ram~42983|combout
8.826        2.096      FF      IC      IMem|ram~42984|datad
9.107        0.281      FF      CELL   IMem|ram~42984|combout
9.334        0.227      FF      IC      IMem|ram~42985|datad
9.459        0.125      FF      CELL   IMem|ram~42985|combout
9.688        0.229      FF      IC      IMem|ram~42996|datad
9.813        0.125      FF      CELL   IMem|ram~42996|combout
13.722       3.909      FF      IC      IMem|ram~42997|datad
14.003       0.281      FF      CELL   IMem|ram~42997|combout
14.231       0.228      FF      IC      IMem|ram~43040|datad
14.381       0.150      FR      CELL   IMem|ram~43040|combout
14.584       0.203      RR      IC      IMem|ram~43041|datad
14.739       0.155      RR      CELL   IMem|ram~43041|combout
15.588       0.849      RR      IC      reggie|mux1|Mux27~12|datad
16.025       0.437      RF      CELL   reggie|mux1|Mux27~12|combout
16.257       0.232      FF      IC      reggie|mux1|Mux27~13|datad
16.538       0.281      FF      CELL   reggie|mux1|Mux27~13|combout
17.288       0.750      FF      IC      reggie|mux1|Mux27~14|datad
17.644       0.356      FF      CELL   reggie|mux1|Mux27~14|combout
17.871       0.227      FF      IC      reggie|mux1|Mux27~15|datad
18.021       0.150      FR      CELL   reggie|mux1|Mux27~15|combout
18.735       0.714      RR      IC      reggie|mux1|Mux27~16|datad
18.890       0.155      RR      CELL   reggie|mux1|Mux27~16|combout
19.093       0.203      RR      IC      reggie|mux1|Mux27~19|datad
19.248       0.155      RR      CELL   reggie|mux1|Mux27~19|combout
20.225       0.977      RR      IC      aluuuu|shifterSel|\G_NBit_MUX:4:MUXI|o_0~0|datad
20.380       0.155      RR      CELL   aluuuu|shifterSel|\G_NBit_MUX:4:MUXI|o_0~0|combout

```

```

20.380 0.155 RR CELL aluuuu|shifterSel|\G_NBit_MUX:4:MUXI|o_0~0|combout
20.647 0.267 RR IC aluuuu|shifter|\phase2:4:mux2|o_0~0|datac
20.914 0.267 RF CELL aluuuu|shifter|\phase2:4:mux2|o_0~0|combout
21.892 0.978 FF IC aluuuu|shifter|\phase2:6:mux2|o_0~0|datab
22.317 0.425 FF CELL aluuuu|shifter|\phase2:6:mux2|o_0~0|combout
22.550 0.233 FF IC aluuuu|shifter|\phase2:6:mux2|o_0~1|datac
22.831 0.281 FF CELL aluuuu|shifter|\phase2:6:mux2|o_0~1|combout
23.602 0.771 FF IC aluuuu|shifter|\phase4:4:mux4|o_0~0|datac
23.883 0.281 FF CELL aluuuu|shifter|\phase4:4:mux4|o_0~0|combout
25.274 1.391 FF IC aluuuu|shifter|\phase4:4:mux4|o_0~1|datad
25.424 0.150 FR CELL aluuuu|shifter|\phase4:4:mux4|o_0~1|combout
25.635 0.211 RR IC aluuuu|shifter|\phase5:4:mux5|o_0~0|datad
25.790 0.155 RR CELL aluuuu|shifter|\phase5:4:mux5|o_0~0|combout
26.017 0.227 RR IC aluuuu|finalMux|Mux27~3|datad
26.172 0.155 RR CELL aluuuu|finalMux|Mux27~3|combout
26.376 0.204 RR IC aluuuu|finalMux|Mux27~4|datad
26.515 0.139 RF CELL aluuuu|finalMux|Mux27~4|combout
29.045 2.530 FF IC DMem|ram~42415|datad
29.468 0.423 FR CELL DMem|ram~42415|combout
30.162 0.694 RR IC DMem|ram~42416|datad
30.301 0.139 RF CELL DMem|ram~42416|combout
31.782 1.481 FF IC DMem|ram~42417|datac
32.063 0.281 FF CELL DMem|ram~42417|combout
32.297 0.234 FF IC DMem|ram~42420|datac
32.578 0.281 FF CELL DMem|ram~42420|combout
32.854 0.276 FF IC DMem|ram~42431|datad
33.278 0.424 FF CELL DMem|ram~42431|combout
33.506 0.228 FF IC DMem|ram~42442|datad
33.631 0.125 FF CELL DMem|ram~42442|combout
35.454 1.823 FF IC DMem|ram~42485|datad
35.579 0.125 FF CELL DMem|ram~42485|combout
35.805 0.226 FF IC DMem|ram~42528|datad
35.955 0.150 FR CELL DMem|ram~42528|combout
36.159 0.204 RR IC DMem|ram~43040|datad
36.314 0.155 RR CELL DMem|ram~43040|combout
36.525 0.211 RR IC whyislboannoyingjesus|Mux0~2|datad
36.680 0.155 RR CELL whyislboannoyingjesus|Mux0~2|combout
37.311 0.631 RR IC whyislboannoyingjesus|Mux0~3|datac
37.596 0.285 RR CELL whyislboannoyingjesus|Mux0~3|combout
37.800 0.204 RR IC whyislboannoyingjesus|Mux0~4|datad
37.939 0.139 RF CELL whyislboannoyingjesus|Mux0~4|combout
38.969 1.030 FF IC manilovedoom2|\G_NBit_MUX:24:MUXI|o_0~5|datac
39.249 0.280 FF CELL manilovedoom2|\G_NBit_MUX:24:MUXI|o_0~5|combout
39.476 0.227 FF IC manilovedoom2|\G_NBit_MUX:24:MUXI|o_0~6|datad
39.601 0.125 FF CELL manilovedoom2|\G_NBit_MUX:24:MUXI|o_0~6|combout
41.909 2.308 FF IC reggie|\g1:12:dff|\regfile:24:reggie|s_Q~feeder|datac
42.190 0.281 FF CELL reggie|\g1:12:dff|\regfile:24:reggie|s_Q~feeder|combout
42.190 0.000 FF IC reggie|\g1:12:dff|\regfile:24:reggie|s_Q|d
42.294 0.104 FF CELL regFile:reggie|registerNbit:\g1:12:dff|dffg:\regfile:24:reggie|s_Q
42.294 0.104 FF CELL regFile:reggie|registerNbit:\g1:12:dff|dffg:\regfile:24:reggie|s_Q
Data Required Path:
Total (ns) Incr (ns) Type Element
-----
20.000 20.000 latch edge time
23.399 3.399 R clock network delay
23.407 0.008 clock pessimism removed
23.387 -0.020 clock uncertainty
23.405 0.018 uTsu regFile:reggie|registerNbit:\g1:12:dff|dffg:\regfile:24:reggie|s_Q
Data Arrival Time : 42.294
Data Required Time : 23.405
Slack : -18.889 (VIOLATED)

```